

Hall Ticket Number:

Y I 9 A C S 4 2 8

I/IV B. Tech (Regular / Supplementary) DEGREE EXAMINATION

November, 2020

Second Semester

Time: Three Hours

Computer Science Engineering

Basic Electrical and Electronics Engineering

Maximum : 50 Marks

Answer ALL Questions from PART-A.

(1X10 = 10 Marks)

Answer ANY FOUR questions from PART-B.

(4X10=40 Marks)

Part - A


(1X10=10 Marks)

1. Answer all questions

- Draw the AC power triangle.
- Write the relation between ' ω ' and ' T ' in a periodic waveform.
- State Norton's Theorem.
- Write the formula for regulation in a transformer.
- Draw the Torque-slip Characteristics of an induction motor.
- Draw the symbol of a Enhancement type MOSFET.
- Define cut-in voltage in a diode.
- Define Clamper and draw the basic Clamper circuit.
- Define pinch off voltage.
- Define CMRR in an Op-amp.

Part - B

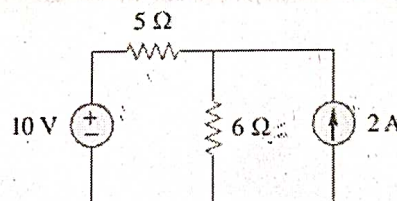- 2.a State Superposition theorem, and for the below circuit determine the current in the 6Ω resistor using superposition theorem. (5M)



- 2.b Explain the relationship between the voltages and currents in series RL and RC elements for AC supply with the help of phasor diagrams. (5M)
- 3.a What is Delta connection, and derive the relationship between line currents and phase currents in a balanced Delta-connection with the help of Phasor diagram. (5M)
- 3.b Define Resonance, and derive the condition for resonance in a series RLC circuit. (5M)
- 4.a Draw the exact equivalent circuit of a transformer referred to primary and derive the expression for overall impedance of the transformer referred to primary. (5M)
- 4.b State the principle on which a DC generator works, Draw the constructional diagram of a DC generator and explain about various parts in it. (5M)
- 5.a What is BH-curve and Explain the significance of the BH-curve in AC machines. (5M)
- 5.b Explain the construction and working of Synchronous generator with a neat sketch. (5M)

P.T.O.

18EE001

- 6.a/ What is a full-wave rectifier? Explain the working of a full-wave rectifier and derive an expression for the RMS value of the output voltage for a sinusoidal wave input. (5M)
- 6.b/ What is a Zener diode and Explain the operation of the Zener-diode as a voltage regulator. (5M)
- 7.a/ Explain the operation of a transistor in CE configuration and draw its input and output characteristics. (5M)
- 7.b/ Explain different modes of operations of a PN junction diode with the help of its VI characteristics. (5M)
- 8.a/ Explain the construction of JFET and draw the input and output characteristics of a JFET in common drain Configuration. (5M)
- 8.b/ Draw the symbol of an ideal Op-amp and write the characteristics of an ideal Op-amp. (5M)
- 9.a/ Derive the expression for the voltage gain of an Op-amp in inverting mode of Operation. (5M)
- 9.b/ Explain with a neat circuit how an Op-amp can be used as an Integrator. (5M)
-